

## Lab Member

Table Number : 7

Section: 2 (Wednesday) ▾


Name	Student Number
Worralop Srichainont	6632200221
Putawan Sratongtuan	6632170021
Pon Kittinaraporn	6630237121
Siwat Sonkadam	6632219221

## Objectives

1. To understand ROM and RAM.
2. To learn how to generate and instantiate ROM and RAM with values.
3. To get familiar with the IP Catalog.

## Read-Only Memory (ROM)


Read-Only Memory (ROM) is non-volatile memory used to store fixed data, such as firmware, look-up tables, or initialization code, that remains intact even when the power is off. ROM is ideal for applications where data does not need to be modified frequently, ensuring reliability and consistency. It works by storing preloaded data in memory cells, which can be read but not altered during normal operation. In FPGA designs, ROM is efficiently implemented using embedded memory blocks, reducing resource usage compared to using registers or flip-flops.

 

**Figure 1: Read-Only Memory (ROM)**

## Random Access Memory (RAM)


Random Access Memory (RAM) is a volatile memory used for temporary data storage, allowing both read and write operations. Like ROM, RAM could be implemented using registers, but this approach is resource-intensive and inefficient. To address this, FPGAs include dedicated memory blocks, such as BlockRAM in Xilinx or Memory Blocks in Altera, providing an efficient and cost-effective way to implement RAM within FPGA designs.

 

**Figure 2: Random Access Memory (RAM)**

## Block RAM

Block RAM (BRAM) is a dedicated memory resource in FPGAs, optimized for efficient memory implementation without using general-purpose logic like CLBs. BRAM sizes range from 10-20 Kbits, with FPGAs containing dozens to thousands of them. In Xilinx, BRAMs can be inferred automatically during synthesis if the HDL code follows specific patterns.

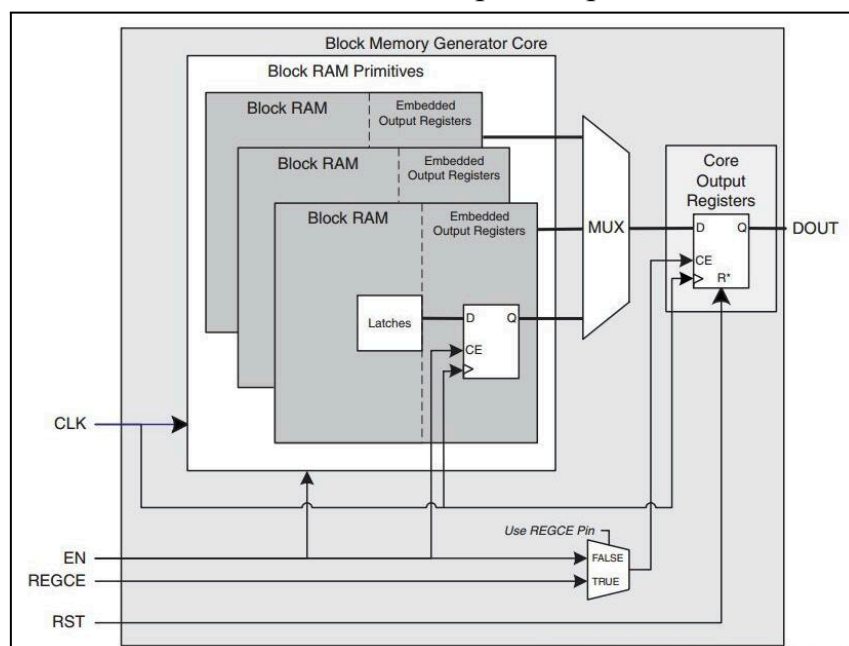

**Figure 3: Block RAM**

## **IP Catalog**


The Xilinx IP Catalog is a feature in Vivado that provides a library of pre-made building blocks, called IP cores, that you can use in your designs. These IP cores save time by letting you use tested and ready-to-use components instead of designing everything from scratch. It's like a toolbox where you can pick and configure parts for your project, such as memory controllers, arithmetic blocks, or communication interfaces.

## Lab Exercise 1

In this exercise, you will implement a BCD converter that reads inputs from 6 binary switches and uses read-only memory (ROM) for converting 6-bit binary to 2-digit BCD for displaying on a seven-segment display.



**Figure 4: Overview Idea of System**

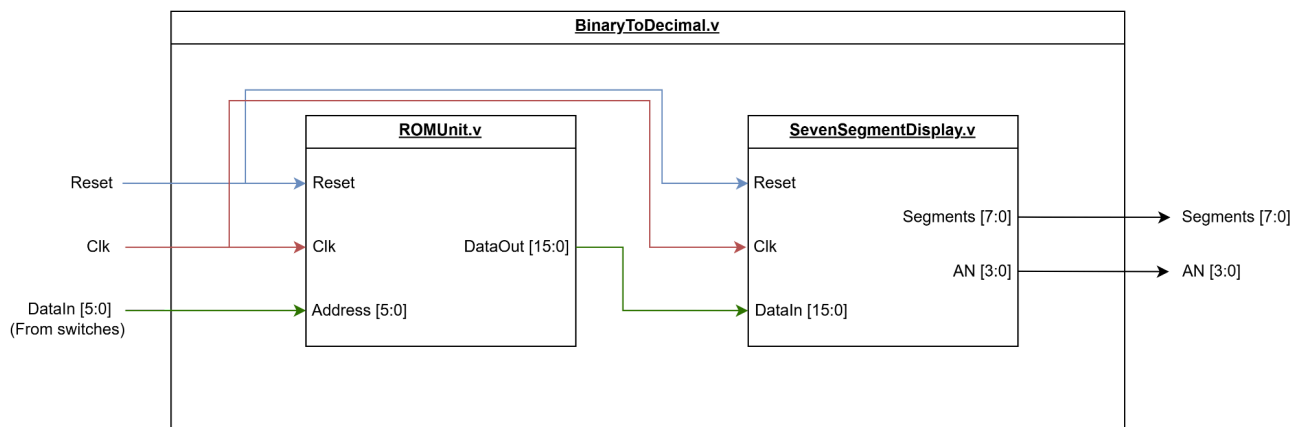

**Figure 5: System Overview**

Figure 5 illustrates the system overview to be implemented in this lab exercise. The system consists of 3 modules, each with a specific role as described below:

1. **BinaryToDecimal**: This is the top-level module responsible for integrating and connecting ROM and SevenSegmentDisplay.
2. **ROMUnit**: The read-only memory which stores 2-digit BCD.
3. **SevenSegmentDisplay**: Displays the value on the 7-segment display.  
This module is already implemented.

## Part 1 : ROM Module

Our read-only memory (ROM) stores 2-digit BCD for each 6-bit binary. Therefore, we must define our ROM as a lookup table in which the address represents 6-bit binary and the output data represents 2-digit BCD.

- The data represents 2-digit BCD, which each digit uses 4 bits. Therefore, the data must be 8 bits.
- For the address, the 6-bit binary number requires  $2^6 = 64$  addressable locations (0 to 63).

Address	Decimal Equivalent	BCD Output
000000	0	0000 0000
000001	1	0000 0001
000010	2	0000 0010
...	...	...
111110	62	0110 0010
111111	63	0110 0011

For our **ROMUnit** module, the module has the following ports:

- **Inputs:**
  - **Reset:** Reset signal.
  - **Clk:** Clock signal for synchronization.
  - **Address:** 6-bit address for looking up in the lookup table.
- **Output:**
  - **DataOut:** 8-bit BCD output data.

## Instruction

1. Create a new project and import all the necessary files from the following source: <https://github.com/2110363-HW-SYN-LAB/lab/tree/main/Lab4>
2. Create a ROM module for storing our BCD data. **Choose one of the following methods** to create ROM module:

### Method 1: Writing your own ROM module

- Create your memory file (.mem file) which will contain data stored in each address. For example, line 1 of the file represents data stored at address 0.

**Hint:** You can read how a .mem file looks like in Lab 4 Guide at “How to initialize ROM value” section (path 1).

- Modify the provided ROMUnit module to initialize the memory and make it work as described above.

**Hint:** You can initialize memory by using `$readmemb(...)` or `$readmemh(...)` functions.

```
// Initialize memory using binary data
$readmemb("<bin_memory_file_name>", memory_array)

// OR

// Initialize memory using hexadecimal data
$readmemh("<hex_memory_file_name>", memory_array)
```

**You can read how to create and initialize memory in Lab 4 Guide at “How to initialize ROM value” section (path 1).**

### Method 2: Generating ROM module using IP Catalog

In case you are lazy at writing modules from scratch, you can generate the modules using IP Catalog. Generate the ROM module using IP Catalog by selecting “**Block Memory Generator**” in IP Catalog

- Make sure that you select the right memory type (Single Port ROM).
- Adjust **port width** (length of each data), **port height** (total number of addressable location), and **enabled port type** correctly in **Port**


**A Options.**

- Adjust the reset signal behavior in **Port A Output Reset Options** in **Port A Options**.
- Initialize the memory in **Memory Initialization** tab in **Other Options**.


Hint: You can read how to generate ROM and initialize memory (.coe file) using IP Catalog in Lab 4 Guide at “How to initialize ROM value” section (path 2).

Submit the evidence of your ROM module.

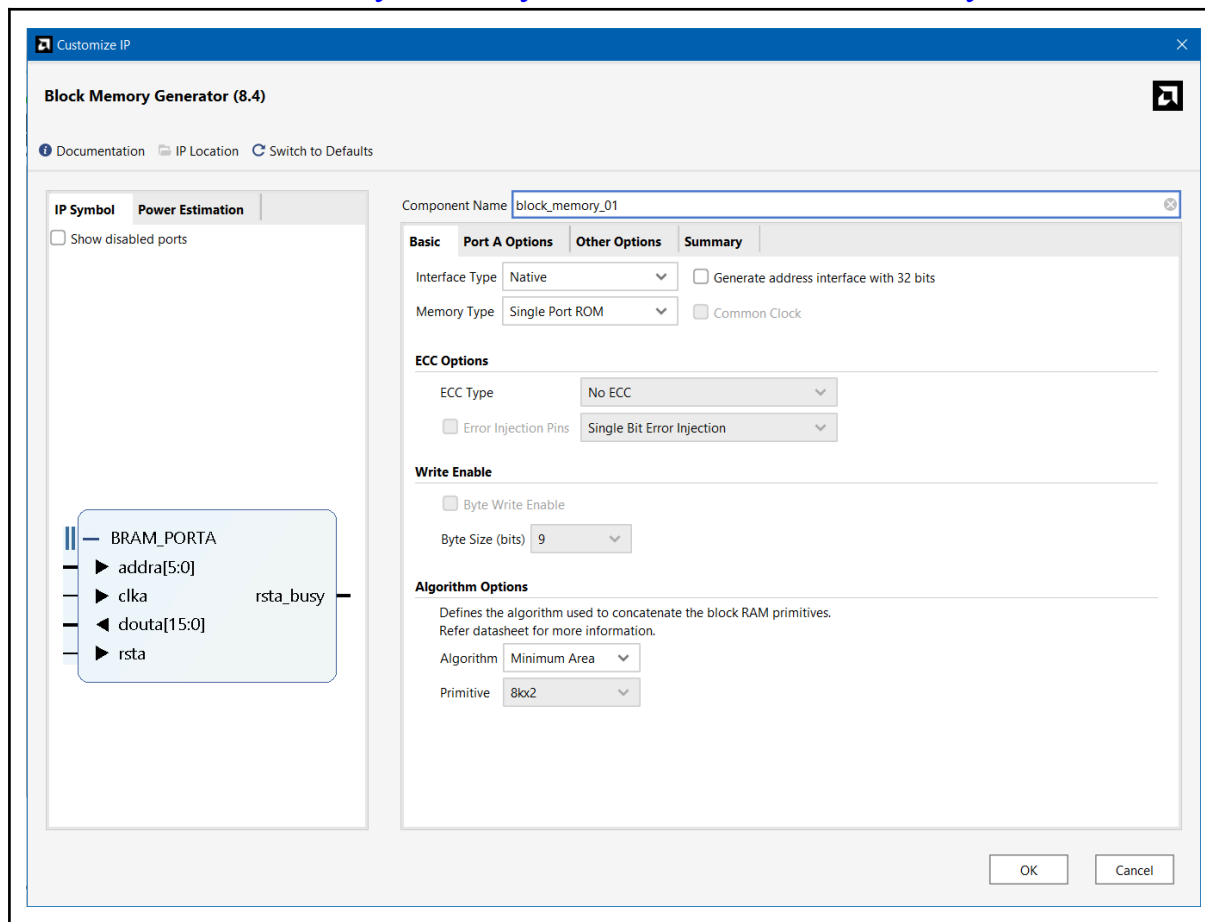- If you write your own ROM module (method 1), paste ROMUnit module code here.
- If you generate ROM module using IP Catalog (method 2), capture the screenshot of IP Symbol of your module in Block Memory Generator.





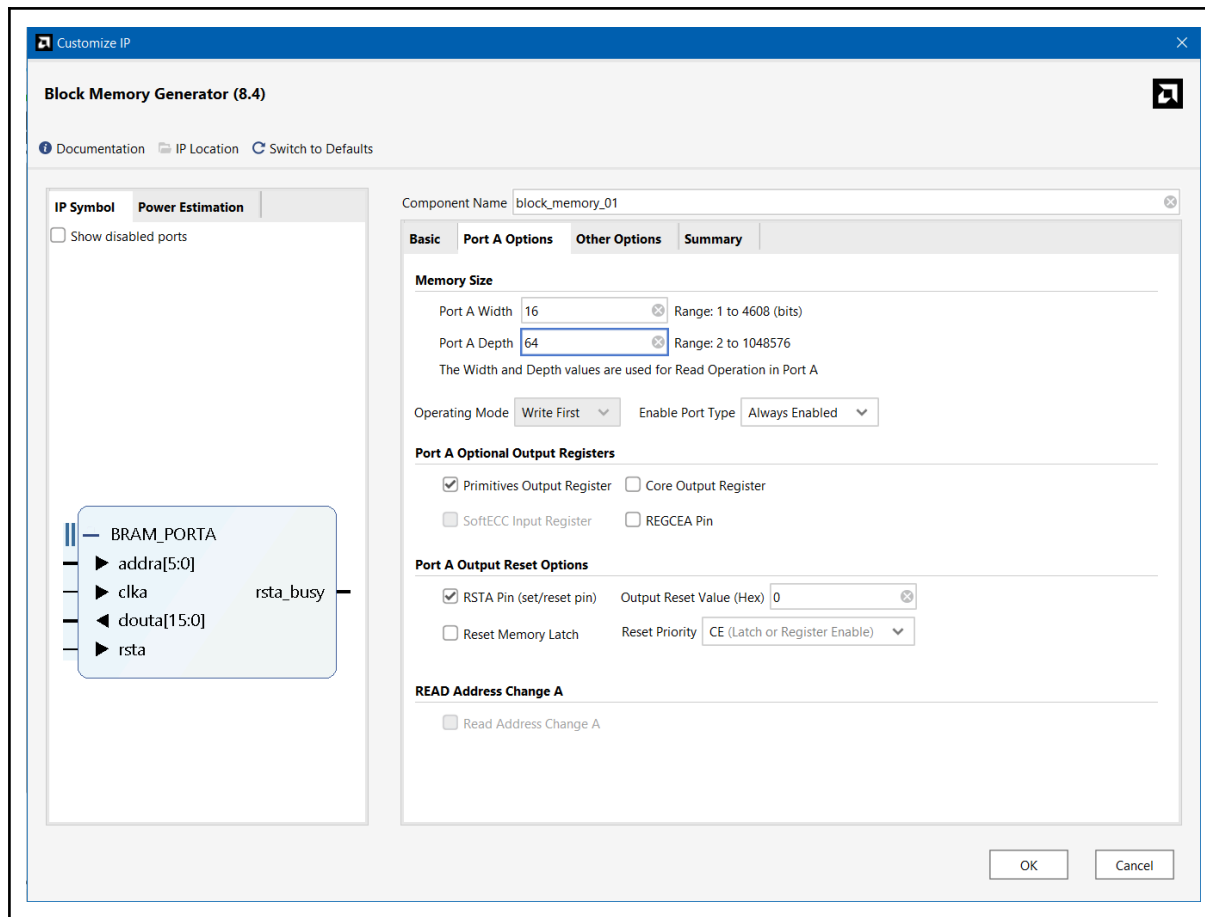

In case you are writing your own ROM module (method 1), run the testbench to verify your ROMUnit module using either Xilinx or CocoTB and capture your testbench result and waveform. (You can skip this if you use IP Catalog)

[If you use CocoTB, don't forget to copy memory file (.mem) and paste inside CocoTB directory]

## Part 2 : Top-level Module and Hardware Programming

Now, we will integrate **ROMUnit** and **SevenSegmentDisplay** modules together such that the output of ROM can be sent to a seven-segment display to show in the Basys3 board.

For the **BinaryToDecimal** module (top-level module), The module has the following ports:

- **Inputs:**
  - **Reset:** Resets the system.
  - **Clk:** Clock signal for synchronization.
  - **DataIn [5:0]:** The 6-bit binary value which will be converted to 2-digit BCD.
- **Output:**
  - **Segments [7:0]:** Signal that is used to control cathode of the 7-segments display.
  - **AN [3:0]:** Signal that is used to control anode of the 7-segments display.

The port mappings from the **BinaryToDecimal** module (top-level module) to Basys3 board are as follows:

BinaryToDecimal ports	Basys3 board
Reset	BTNC
Clk	Basys3 100Mhz Clk
DataIn [5:0]	{SW5, SW4, SW3, SW2, SW1, SW0}
AN [3:0]	{AN3, AN2, AN1, AN0}
Segments [7:0]	{CA, CB, CC, CD, CE, CF, CG, DP}

### Instruction

1. According to Figure 4 and 5, integrate both **ROMUnit** and **SevenSegmentDisplay** modules together in the **BinaryToDecimal** module (top-level module).

Insert your modified BinaryToDecimal module here.

```
module BinaryToDecimal (
    input wire      Clk,
    input wire      Reset,
    input wire [5:0] DataIn,
    output wire [7:0] Segments,
    output wire [3:0] AN
);
    // Add your code here
    wire [15:0] BCDoutput;
    block_memory_01 block_memory_01_inst(
        .rsta(Reset),
        .clka(Clk),
        .addra(DataIn),
        .douta(BCDoutput)
    );
    SevenSegmentDisplay SevenSegmentDisplay_inst(
        .Reset(Reset),
        .Clk(Clk),
        .DataIn(BCDoutput),
        .Segments(Segments),
        .AN(AN)
    );
    // End of your code
endmodule
```

2. From the table above, complete this mapping table below to map your system's inputs and outputs onto the Basys3 pins.

Hint #1: Look up the [Basys3 reference manual](#) on page 7 and 15.

Hint #2: Many pin mappings are similar to Lab 1-3 exercises.

Complete the mapping table.

Top-level module input/output	Basys3 Pins
Reset	U18
Clk	W5
DataIn[0]	V17
DataIn[1]	V16
DataIn[2]	W16
DataIn[3]	W17
DataIn[4]	W15
DataIn[5]	V15
AN[0]	U2
AN[1]	U4
AN[2]	V4
AN[3]	W4
Segments[0]	V7
Segments[1]	U7
Segments[2]	V5
Segments[3]	U5
Segments[4]	V8
Segments[5]	U8
Segments[6]	W6
Segments[7]	W7

3. Create the constraint file.

[Submit your constraint file here.](#)

```
set_property BITSTREAM.GENERAL.COMPRESS TRUE [current_design]
set_property BITSTREAM.CONFIG.CONFIGRATE 33 [current_design]
```

```
set_property CONFIG_MODE SPIx4 [current_design]

set_property IOSTANDARD LVCMOS33 [get_ports {DataIn[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {DataIn[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {DataIn[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {DataIn[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {DataIn[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {DataIn[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports Clk]
set_property IOSTANDARD LVCMOS33 [get_ports Reset]
set_property IOSTANDARD LVCMOS33 [get_ports {AN[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {AN[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {AN[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {AN[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segments[7]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segments[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segments[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segments[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segments[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segments[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segments[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segments[0]}]
set_property PACKAGE_PIN V15 [get_ports {DataIn[5]}]
set_property PACKAGE_PIN W15 [get_ports {DataIn[4]}]
set_property PACKAGE_PIN W17 [get_ports {DataIn[3]}]
set_property PACKAGE_PIN W16 [get_ports {DataIn[2]}]
set_property PACKAGE_PIN V16 [get_ports {DataIn[1]}]
set_property PACKAGE_PIN V17 [get_ports {DataIn[0]}]
set_property PACKAGE_PIN W5 [get_ports Clk]
set_property PACKAGE_PIN U18 [get_ports Reset]
set_property PACKAGE_PIN W4 [get_ports {AN[3]}]
set_property PACKAGE_PIN V4 [get_ports {AN[2]}]
set_property PACKAGE_PIN U4 [get_ports {AN[1]}]
set_property PACKAGE_PIN U2 [get_ports {AN[0]}]
set_property PACKAGE_PIN W7 [get_ports {Segments[7]}]
set_property PACKAGE_PIN W6 [get_ports {Segments[6]}]
set_property PACKAGE_PIN U8 [get_ports {Segments[5]}]
set_property PACKAGE_PIN V8 [get_ports {Segments[4]}]
set_property PACKAGE_PIN U5 [get_ports {Segments[3]}]
set_property PACKAGE_PIN V5 [get_ports {Segments[2]}]
set_property PACKAGE_PIN U7 [get_ports {Segments[1]}]
set_property PACKAGE_PIN V7 [get_ports {Segments[0]}]
```


```
create_clock -period 10.000 -name Clk -waveform {0.000 5.000} [get_ports Clk]
```

4. Run the synthesis.
5. Run the implementation, generate the bitstream, and program the **Basys3** device.
6. **[Checkpoint]** Call TA to inspect your work.

## Lab Exercise 2


In this exercise, we will design and build a circuit to work as a **Stack** (LIFO). The user can use two push buttons in order to PUSH or POP. We will use 8 switches on the board as a value. When the user hits a PUSH button, it will store the value from the switches to the stack. When the user hits the POP switch, it will display the popped value in the 2 hexadecimal digits on the left of a seven-segment display. The other 2 right digits in the seven-segment display are used to display the number of elements currently in the stack.

- The stack can keep up to 256 elements.
- If the stack is empty, hitting POP should not do anything.
- If the stack is full, hitting PUSH should not do anything.
- Pressing the RESET button will reset the stack and system.

 


**Figure 6: Example of Seven-segment Display in System**

Figure 7 shows the example of pushing and popping elements into the stack. Note that the 2 left digits of the seven-segment display will be changed only when the stack is popped.

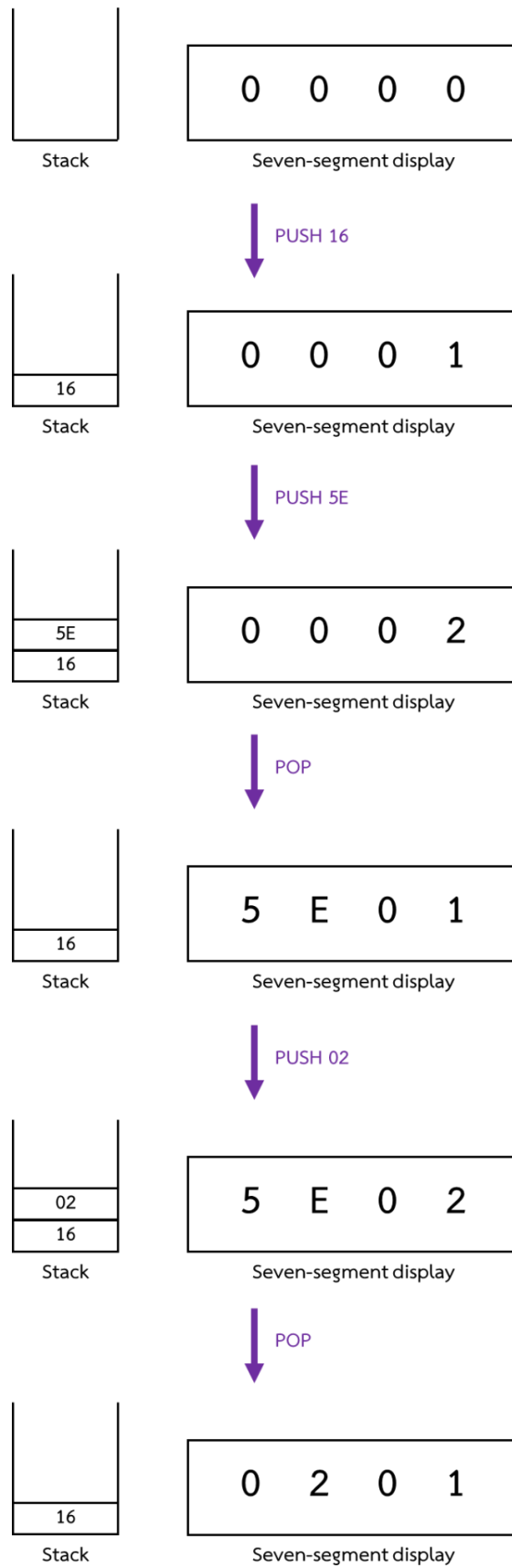
**Figure 7: Example of Pushing and Popping Elements**



For our design, which is shown in Figure 8, we will sanitize the signals from buttons (PUSH and POP signal) then feed these signals with inputs from switches to a stack unit, which will handle operations in stack. In addition, the data from the stack unit will be fed to a seven-segment display to show the number of elements and the latest popped value of our stack.

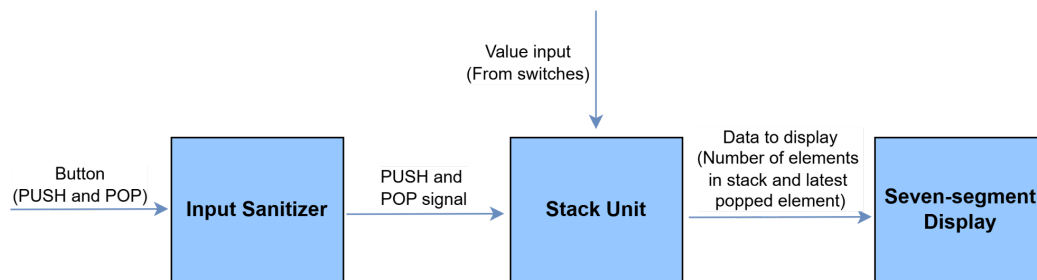

**Figure 8: Overview Idea of System**

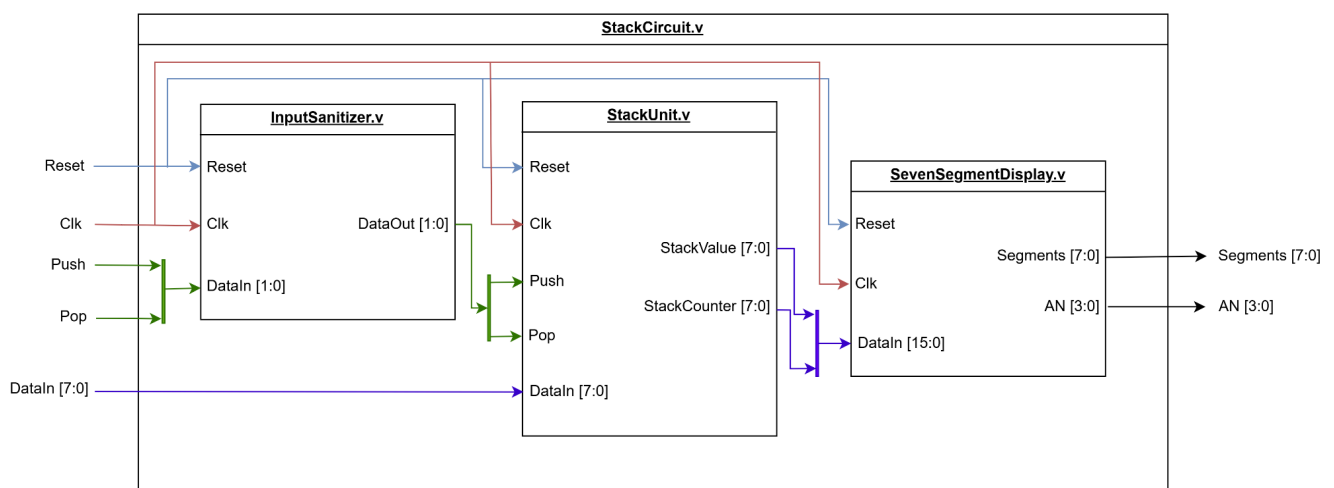

**Figure 9: System Overview**

Figure 9 illustrates the system overview in this lab exercise. The system consists of 4 main modules, each with a specific role as described below:


1. **StackCircuit**: This is the top-level module responsible for integrating and connecting input sanitizer, stack unit, and seven-segment display.
2. **InputSanitizer**: Module which eliminates noise and generates a clean single pulse.
3. **StackUnit**: Module which performs operations and stores elements of stack.
4. **SevenSegmentDisplay**: Displays the value on the 7-segment display.

## Part 1 : Stack Module

First, we will implement the stack module which will perform operations and store elements of stack.

- The module must have something which can store elements for our stack, which we will use random-access memory (RAM) to be the data storage.
- When PUSH signal are triggered, element must be added into RAM.
- When POP signal are triggered, last element must be removed from RAM.
- When RESET signal are triggered, all data in RAM must be cleared and everything must be reset.

In the design (Figure 10), **StackController.v** module has responsibility for controlling all logic about stack, and **RAMUnit.v** has responsibility for element storage for our stack.

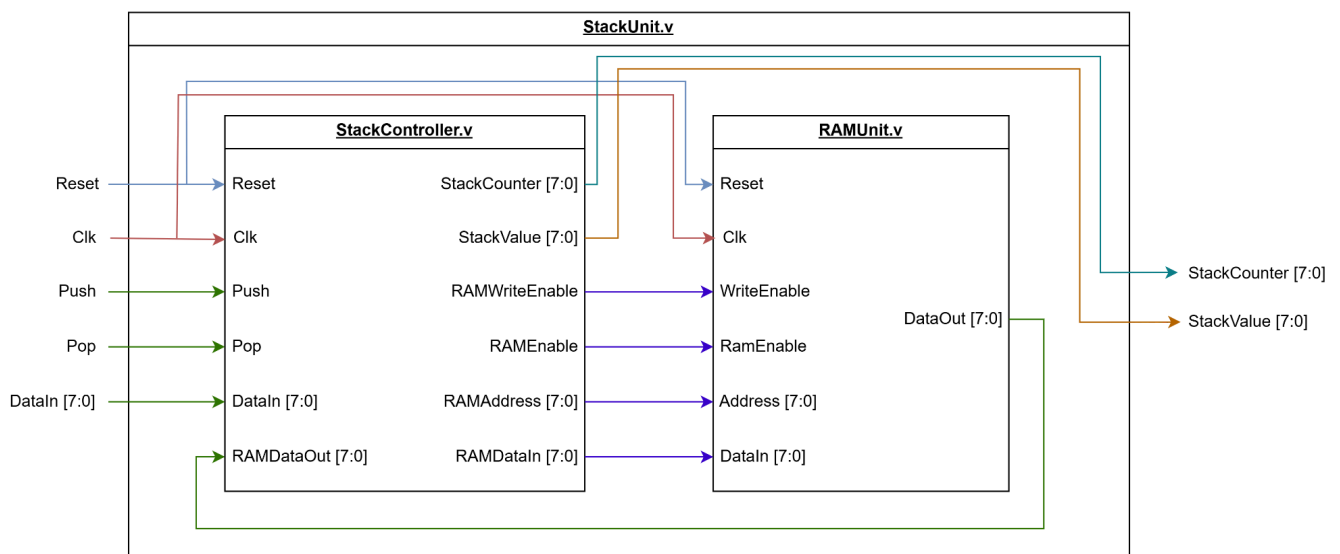

**Figure 10: Design of StackUnit**

## Part 1.1 : RAM Module

We must implement a RAM module to store our elements in the stack.  
Our requirements are:

- The RAM module shall store 256 elements for the stack.
- Each element can be represented as 8-bit value or 2-hexadecimal digits.

### Instruction

1. Create a RAM module to be our data storage for the stack. **Choose one of the following methods** to create RAM module:

#### Method 1: Writing your own RAM module

Modify the provided RAMUnit module to initialize the memory and make it work as described above.

**Hint:** You can read how RAM actually works in the Lab 4 Guide at the “RAM behavior” section.

#### Method 2: Generating RAM module using IP Catalog

In case you are lazy at writing RAM from scratch, you can generate the modules using IP Catalog. Generate the RAM module using IP Catalog by selecting “**Block Memory Generator**” in IP Catalog

- Make sure that you select the right memory type (Single Port RAM).
- Adjust **port write/read width** (length of each data), **port write/read height** (total number of addressable location), and **enabled port type** correctly in **Port A Options**.
- Select **Primitives Output Register**.
- Ensure that **RSTA Pin** is enabled, **Output Reset Value** is 0, and **Reset Priority** is CE (Latch or Register Enable).

**Hint:** You can read how to generate RAM using IP Catalog in Lab 4 Guide at “Random-Access Memory” section.

Submit the evidence of your RAM module.

- If you write your own RAM module (method 1), paste RAMUnit module code here.
- If you generate a RAM module using IP Catalog (method 2), capture the screenshot of IP Symbol of your module in Block Memory Generator.

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
/////////////////////////////////////////////////////////////////
// Create Date: 01/16/2025 01:45:27 AM
// Design Name: StackCircuit
// Module Name: RAMUnit
// Project Name: StackCircuit
// Target Devices: Basys3
// Tool Versions: 2023.2
// Description: Handle storing Data in the RAM
/////////////////////////////////////////////////////////////////
/////////////////////////////////////////////////////////////////

module RAMUnit (
    input wire      Clk,          // Clock signal
    input wire      Reset,        // Reset signal (active high)
    input wire      WriteEnable,  // Write enable (active high)
    input wire      RamEnable,    // RAM enable (active high)
    input wire [7:0] Address,     // 8-bit Address input
    input wire [7:0] DataIn,      // 8-bit Data input
    output reg [7:0] DataOut      // 8-bit Data output
);

    // 8-bit memory with 256 locations
    reg [7:0] mem [0:255];

    // Declare 'i' outside the always block:
    integer i;

    // Synchronous process for Reset, Read, and Write
    always @(posedge Clk) begin
        if (Reset) begin
            // Synchronously clear the memory to 0
            for (i = 0; i < 256; i = i + 1) begin
                mem[i] <= 8'b00000000;
            end
        end
    end
endmodule
```

```

        DataOut <= 8'b00000000;
    end

    else if (RamEnable) begin
        if (WriteEnable) begin
            mem[Address] <= DataIn;
            DataOut <= DataIn;
        end
        else begin
            DataOut <= mem[Address];
        end
    end
end

end

// For waveform dumping in COCOTB simulation
`ifdef COCOTB_SIM
initial begin
    $dumpfile("waveform.vcd"); // Name of the dump file
    $dumpvars(0, RAMUnit);     // Dump all variables for the top
module
end
`endif

endmodule

```

In case you are writing your own RAM module (method 1), run the testbench to verify your RAMUnit module using either Xilinx or CocoTB and capture your testbench result and waveform. (You can skip this if you use IP Catalog)

```

(cocotb) D:\Lab4\Exercise2\Exercise2\cocotb\RAMUnitTB>make
rm -f results.xml
"make" -f Makefile results.xml
make[1]: Entering directory '/d/Lab4/Exercise2/Exercise2/cocotb/RAMUnitTB'
/c/iverilog/bin/iverilog -o sim_build/sim.vvp -D COCOTB_SIM=1 -s RAMUnit -g2012 -f sim_build/cmds.f /d/Lab4/Exercise2/Exercise2/cocotb/RAMUnitTB/../../src/
RAMUnit.v
rm -f results.xml
MODULE=TB TESTCASE= TOPLEVEL=RAMUnit TOPLEVEL_LANG=verilog \
  /c/iverilog/bin/vvp -M C:/Users/jjab6/miniconda3/envs/cocotb/lib/site-packages/cocotb/libs -m cocotbvpi_icarus sim_build/sim.vvp
nt. Using system-wide Python interpreter
0.00ns INFO gpi ..\gpi\GpiCommon.cpp:81 in set_program_name_in_venv Did not detect Python virtual environme
0.00ns INFO gpi ..\gpi\GpiCommon.cpp:101 in gpi_print_registered_impl VPI registered
0.00ns INFO cocotb Running on Icarus Verilog version 12.0 (devel)
0.00ns INFO cocotb Running tests with cocotb v1.9.2 from C:/Users/jjab6/miniconda3/envs/cocotb/lib/site-packages/cocotb
0.00ns INFO cocotb Seeding Python random module with 1738744021
0.00ns INFO cocotb.regression Found test TB.RAMUnitTB
0.00ns INFO cocotb.regression running RAMUnitTB (1/1)
0.00ns INFO cocotb.RAMUnit Try accessing the design.
VCD info: dumpfile waveform.vcd opened for output.
770.00ns INFO cocotb.RAMUnit Running test!
770.00ns INFO cocotb.regression Test Complete
770.00ns INFO cocotb.regression RAMUnitTB passed
*****
** TEST STATUS SIM TIME (ns) REAL TIME (s) RATIO (ns/s) **
** TB.RAMUnitTB PASS 770.00
*****
** TESTS=1 PASS=1 FAIL=0 SKIP=0 770.00
*****
make[1]: Leaving directory '/d/Lab4/Exercise2/Exercise2/cocotb/RAMUnitTB'
(cocotb) D:\Lab4\Exercise2\Exercise2\cocotb\RAMUnitTB>

```



## Part 1.2 : StackController

It's time to implement the heart of our system, the StackController module. This module will perform every logic about stack such as pushing and popping elements in stack. Remind that our requirements are:

- When PUSH signal are triggered, element must be added into RAM.
- When POP signal are triggered, last element must be removed from RAM.
- When RESET signal are triggered, all data in RAM must be cleared and everything must be reset.
- The number of elements in the stack and the latest popped element must be returned, so that we can feed these values to a seven-segment display.

### Instruction

1. From the requirements above, discuss in your group about the idea for implementing this **StackController** module (e.g. how can we retrieve the top element of stack, how to push and pop element, ...).

Hint: If you are not familiar with stack or you are stuck on something here, you can find some ideas by watching [this video](#) or reading Lab 4 Guide at “Stack from RAM” section.

Write down your idea for implementing StackController briefly.

The StackController manages a stack using external RAM with push and pop operations

2. From your idea, implement this module by modifying the **StackController** module.

Insert your modified StackController module here.

```
`timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////
// Create Date: 01/16/2025 01:45:42 AM
// Design Name: StackCircuit
// Module Name: StackController
// Project Name: StackCircuit
// Target Devices: Basys3
```

```
// Tool Versions: 2023.2
// Description: This module is used to implement the stack using a
RAMUnit.
////////////////////////////////////
////////////////////////////////////

module StackController (
    input  wire      Push,          // Push signal (adds element to
stack)
    input  wire      Pop,           // Pop signal (removes element
from stack)
    input  wire      Clk,           // Clock signal
    input  wire      Reset,         // Reset signal (clears stack)
    input  wire [7:0] DataIn,        // Data input for push operation
    input  wire [7:0] RAMDataOut,    // Data read from RAM
    output reg  [7:0] StackCounter,  // Number of elements in the
stack
    output reg  [7:0] StackValue,    // Last popped value
    output reg      RAMWriteEnable,  // Controls RAM write operation
    output reg      RAMEnable,      // Enables RAM operation
    output reg  [7:0] RAMAddress,    // Address for RAM read/write
    output reg  [7:0] RAMDataIn     // Data to write into RAM
);

    // Synchronous process for stack operations
    always @(posedge Clk) begin
        if (Reset) begin
            // Reset everything
            StackCounter  <= 8'b0;  // Reset stack count
            StackValue    <= 8'b0;  // Reset last popped value
            RAMWriteEnable <= 1'b0;  // Disable writing
            RAMEnable     <= 1'b1;  // Keep RAM enabled
        end
        else if (Push && StackCounter == 255) begin
            StackCounter <= StackCounter;
            RAMAddress   <= StackCounter;
            RAMDataIn    <= DataIn;
            RAMWriteEnable <= 1'b1;
        end
        else if (Push && StackCounter < 255) begin
            StackCounter <= StackCounter + 1'b1;
            RAMAddress   <= StackCounter;
        end
    end
endmodule
```



```

        RAMDataIn      <= DataIn;
        RAMWriteEnable <= 1'b1;
    end
    else if (Pop && RAMAddress == 255 && StackCounter == 255)
begin
        // Pop operation: Retrieve last pushed value from RAM
        RAMAddress      <= RAMAddress - 1 ;
        StackValue      <= RAMDataOut;
        StackCounter    <= StackCounter;
        RAMWriteEnable <= 1'b0;
        RAMEnable       <= 1'b1;
    end
    else if (Pop && StackCounter == 1) begin
        // Pop operation: Retrieve last pushed value from RAM
        RAMAddress      <= 0 ;
        StackValue      <= RAMDataOut;
        StackCounter    <= StackCounter - 1;
        RAMWriteEnable <= 1'b0;
        RAMEnable       <= 1'b1;
    end
    else if (Pop && StackCounter > 1) begin
        // Pop operation: Retrieve last pushed value from RAM
        RAMAddress      <= StackCounter - 2;
        StackValue      <= RAMDataOut;
        StackCounter    <= StackCounter - 1;
        RAMWriteEnable <= 1'b0;
        RAMEnable       <= 1'b1;
    end
    else begin
        // Default state: No operations, disable RAM write
        RAMWriteEnable <= 1'b0;
        RAMEnable      <= 1'b1;
    end
end

// For waveform dumping in COCOTB simulation
`ifdef COCOTB_SIM
initial begin
    $dumpfile("waveform.vcd");           // Name of the dump file
    $dumpvars(0, StackController);       // Dump all variables in
this module
end

```

```
`endif  
  
endmodule
```

3. [Optional] Create a testbench (StackControllerTB in cocotb/StackController/TB.py) for the StackController Module. Your testbench must perform all possible operations of the stack. You can use either Xilinx or CocoTB.

Insert your testbench here.

4. [Optional] Run your testbench to verify your module.

Insert your testbench result here.

Insert your testbench waveform here.

## Part 2 : Top-level Module and Hardware Programming

You are almost done. Last thing we will do is to integrate all modules together in the top-level module.

For the **StackCircuit** module (top-level module), The module has the following ports:

- **Inputs:**
  - **Reset:** Resets the system.
  - **Clk:** Clock signal for synchronization.
  - **Push:** Signal for pushing input into stack.
  - **Pop:** Signal for popping the top elements of the stack.
  - **DataIn [7:0]:** The 8-bit binary value which will be input of the stack when pushing.
- **Output:**
  - **Segments [7:0]:** Signal that is used to control cathode of the 7-segments display.
  - **AN [3:0]:** Signal that is used to control anode of the 7-segments display.

The port mappings from the **StackCircuit** module (top-level module) to Basys3 board are as follows:

StackCircuit ports	Basys3 board
Reset	BTNC
Clk	Basys3 100Mhz Clk
Push	BTNR
Pop	BTNL
DataIn [7:0]	{SW7, SW6, SW5, SW4, SW3, SW2, SW1, SW0}
AN [3:0]	{AN3, AN2, AN1, AN0}
Segments [7:0]	{CA, CB, CC, CD, CE, CF, CG, DP}

## Instruction

1. In the **StackUnit**, wire up **RAM** and **StackController** together according to Figure 10. In the other word, complete **StackUnit** module.

[Insert your modified StackUnit module here.](#)

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
/////////////////////////////////////////////////////////////////
// Create Date: 01/16/2025 01:45:55 AM
// Design Name: StackCircuit
// Module Name: StackUnit
// Project Name: StackCircuit
// Target Devices: Basys3
// Tool Versions: 2023.2
// Description: The Module that implement the Stack
/////////////////////////////////////////////////////////////////
/////////////////////////////////////////////////////////////////

module StackUnit (
    input wire Clk,
    input wire Reset,
    input wire [7:0] DataIn,
    input wire Push,
    input wire Pop,
    output wire [7:0] StackValue,
    output wire [7:0] StackCounter
);
    // Add your code here
    wire RAMWriteEnableOutput , RAMEnableOutput ;
    wire [7:0] RAMAddressOutput ;
    wire [7:0] RAMDataInOutOutput ;
    wire [7:0] DataOutOutput ;

    StackController StackControllerInst (
        .Push (Push) ,
        .Pop (Pop) ,
        .Clk (Clk) ,
        .Reset (Reset) ,
        .DataIn (DataIn) ,
        .RAMDataOut (DataOutOutput) ,
        .StackCounter (StackCounter) ,
```



```

    input  wire      Clk,
    input  wire      Reset,
    input  wire      Push,
    input  wire      Pop,
    input  wire [7:0] DataIn,
    output wire [7:0] Segments,
    output wire [3:0] AN
);
    // Add your code here

    wire [1:0] InputSanitizerDataoutOutput ;
    wire [7:0] StackValueOutput ;
    wire [7:0] StackCounterOutput ;

    InputSanitizer InputSanitizerInst (
        .Reset (Reset) ,
        .Clk (Clk) ,
        .DataIn ({Push , Pop}) ,
        .DataOut (InputSanitizerDataoutOutput)
    ) ;

    StackUnit StackUnitInst (
        .Reset (Reset) ,
        .Clk (Clk) ,
        .Push (InputSanitizerDataoutOutput[1]) ,
        .Pop (InputSanitizerDataoutOutput[0]) ,
        .DataIn (DataIn) ,
        .StackValue (StackValueOutput) ,
        .StackCounter (StackCounterOutput)
    );

    SevenSegmentDisplay SevenSegmentDisplayInst (
        .Reset (Reset) ,
        .Clk (Clk) ,
        .DataIn ({StackValueOutput , StackCounterOutput}) ,
        .Segments (Segments) ,
        .AN (AN)
    );
    // End of your code
endmodule

```

3. Map your system's inputs and outputs onto the Basys3 pins, then create a

constraint file.

Hint: Look up the [Basys3 reference manual](#) on page 7 and 15.

[Submit your constraint file here.](#)

```
set_property PACKAGE_PIN U18 [get_ports Reset]
set_property PACKAGE_PIN W5 [get_ports Clk]
set_property PACKAGE_PIN T17 [get_ports Push]
set_property PACKAGE_PIN W19 [get_ports Pop]

set_property PACKAGE_PIN V17 [get_ports {DataIn[0]}]
set_property PACKAGE_PIN V16 [get_ports {DataIn[1]}]
set_property PACKAGE_PIN W16 [get_ports {DataIn[2]}]
set_property PACKAGE_PIN W17 [get_ports {DataIn[3]}]
set_property PACKAGE_PIN W15 [get_ports {DataIn[4]}]
set_property PACKAGE_PIN V15 [get_ports {DataIn[5]}]
set_property PACKAGE_PIN W14 [get_ports {DataIn[6]}]
set_property PACKAGE_PIN W13 [get_ports {DataIn[7]}]

set_property PACKAGE_PIN U2 [get_ports {AN[0]}]
set_property PACKAGE_PIN U4 [get_ports {AN[1]}]
set_property PACKAGE_PIN V4 [get_ports {AN[2]}]
set_property PACKAGE_PIN W4 [get_ports {AN[3]}]

# Updated pin assignments for Segments
set_property PACKAGE_PIN V7 [get_ports {Segments[0]}]
set_property PACKAGE_PIN U7 [get_ports {Segments[1]}]
set_property PACKAGE_PIN V5 [get_ports {Segments[2]}]
set_property PACKAGE_PIN U5 [get_ports {Segments[3]}]
set_property PACKAGE_PIN V8 [get_ports {Segments[4]}]
set_property PACKAGE_PIN U8 [get_ports {Segments[5]}]
set_property PACKAGE_PIN W6 [get_ports {Segments[6]}]
set_property PACKAGE_PIN W7 [get_ports {Segments[7]}]

# Set IOSTANDARD for all pins
set_property IOSTANDARD LVCMOS33 [get_ports Reset]
set_property IOSTANDARD LVCMOS33 [get_ports Clk]
set_property IOSTANDARD LVCMOS33 [get_ports Push]
set_property IOSTANDARD LVCMOS33 [get_ports Pop]
set_property IOSTANDARD LVCMOS33 [get_ports {DataIn[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {DataIn[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {DataIn[2]}]
```

```
set_property IOSTANDARD LVCMOS33 [get_ports {DataIn[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {DataIn[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {DataIn[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {DataIn[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports {DataIn[7]}]

set_property IOSTANDARD LVCMOS33 [get_ports {AN[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {AN[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {AN[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {AN[3]}]

# Updated IOSTANDARD assignments for Segments
set_property IOSTANDARD LVCMOS33 [get_ports {Segments[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segments[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segments[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segments[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segments[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segments[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segments[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Segments[7]}]
```

4. Run the synthesis.
5. Run the implementation, generate the bitstream, and program the **Basys3** device.
6. [\[Checkpoint\]](#) Call TA to inspect your work.